


**THREE PHASE FULLY CONTROLLED AND HALF  
CONTROLLED BRIDGE RECTIFIER**

**Aim:**


To simulate three phase fully controlled and half controlled bridge rectifier.

**Software Used:**

Matlab – Simulink

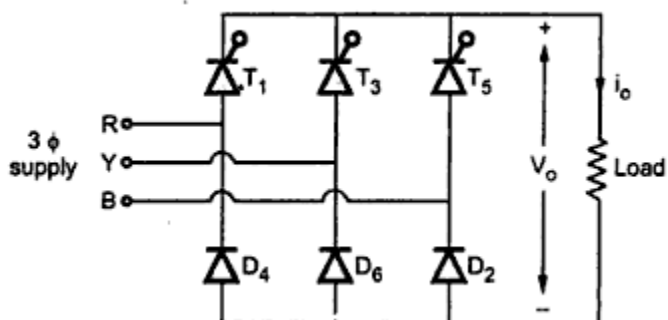
**Circuit Diagram:**

*Fig 1: Three Phase Half Controlled Bridge rectifier*

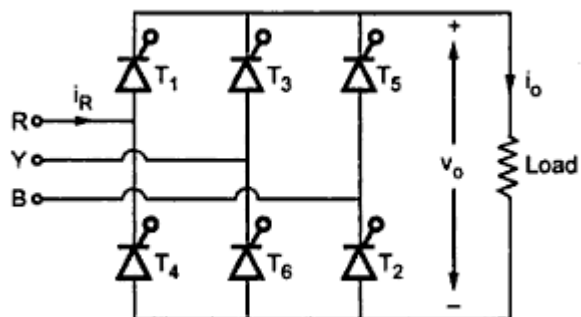


*Fig 2: Three Phase Fully Controlled Bridge rectifier*

**Simulink Models:**

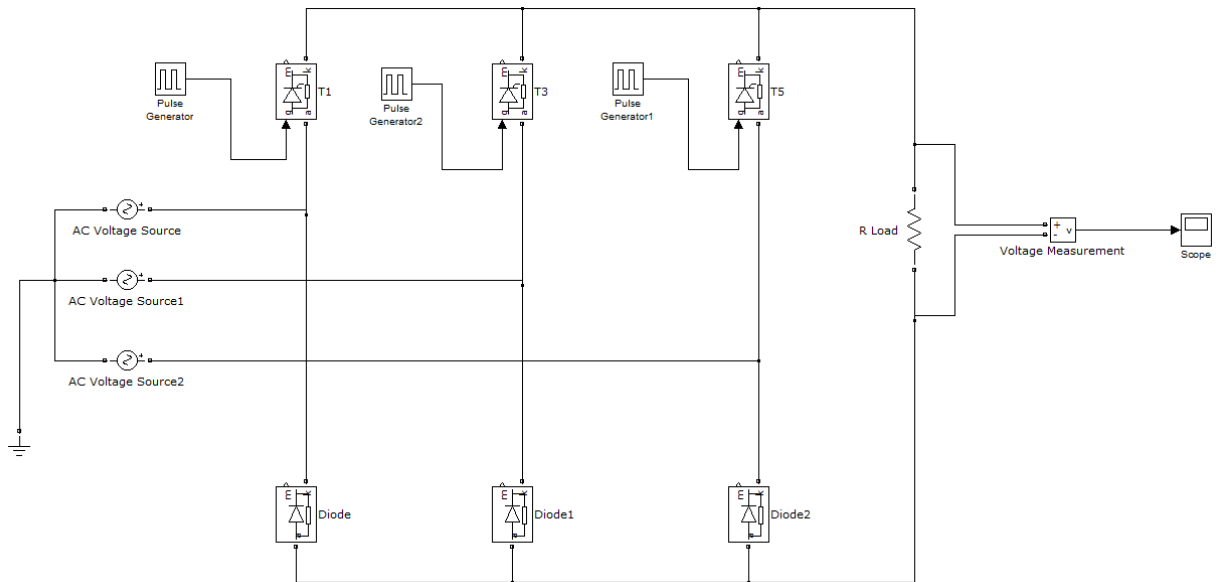


*Fig: Three Phase Half Controlled Rectifier*

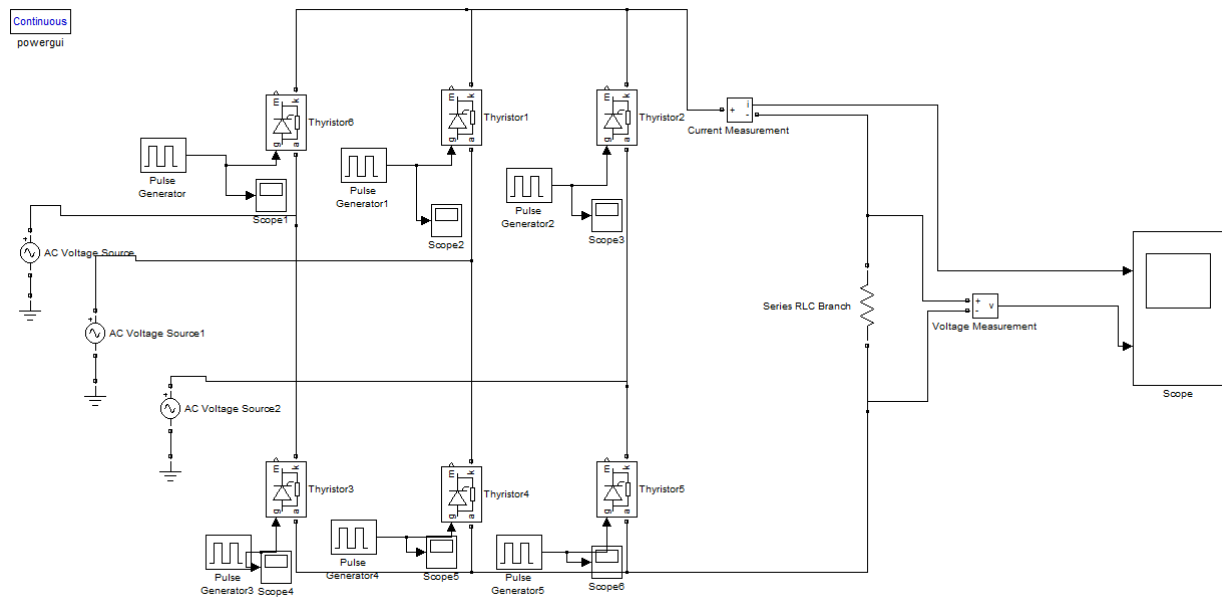

*Fig: Three Phase Fully Controlled Rectifier*
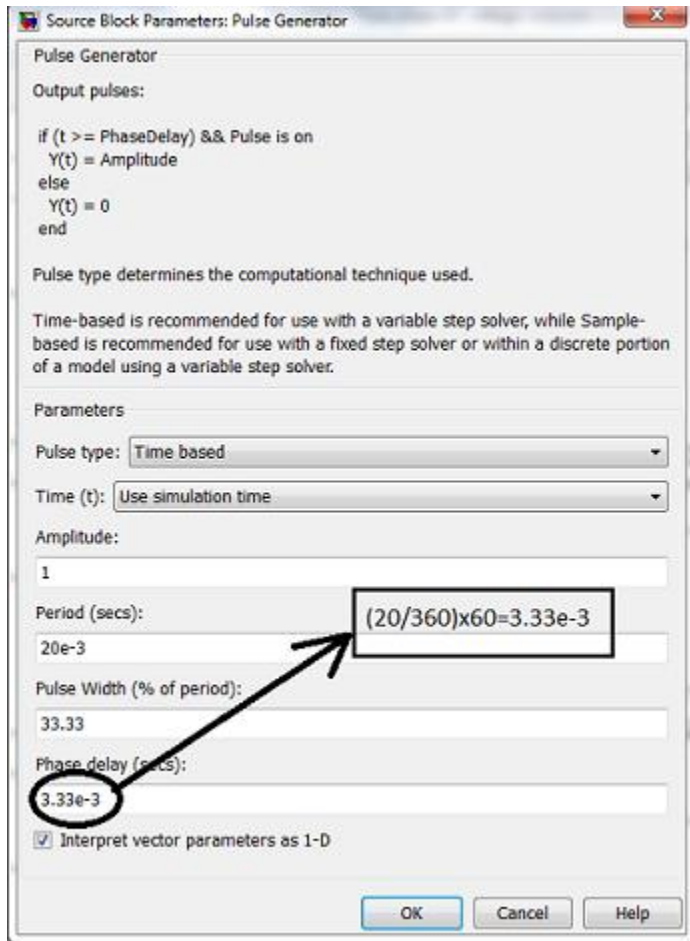
## Entering Firing Angle Values:

In order to trigger thyristors we have to give proper triggering pulses to it using a pulse generator. We can enter values in the box which is obtained by double clicking pulse generator. It's shown in the following figure.



**Complete Triggering Values****For Half controlled Rectifier:**

	<b><u>Firing Angle in degree</u></b>	<b><u>Firing Angle in sec</u></b>
<b>T1</b>	30	1.66e-3
<b>T3</b>	150	8.33e-3
<b>T5</b>	270	15e-3

**For Half controlled Rectifier:**

	<b><u>Firing Angle in degree</u></b>	<b><u>Firing Angle in sec</u></b>
<b>T1</b>	30	1.66e-3
<b>T2</b>	90	5e-3
<b>T3</b>	150	8.33e-3
<b>T4</b>	210	11.66e-3
<b>T5</b>	270	15e-3
<b>T6</b>	330	18.33e-3

**Graphs**

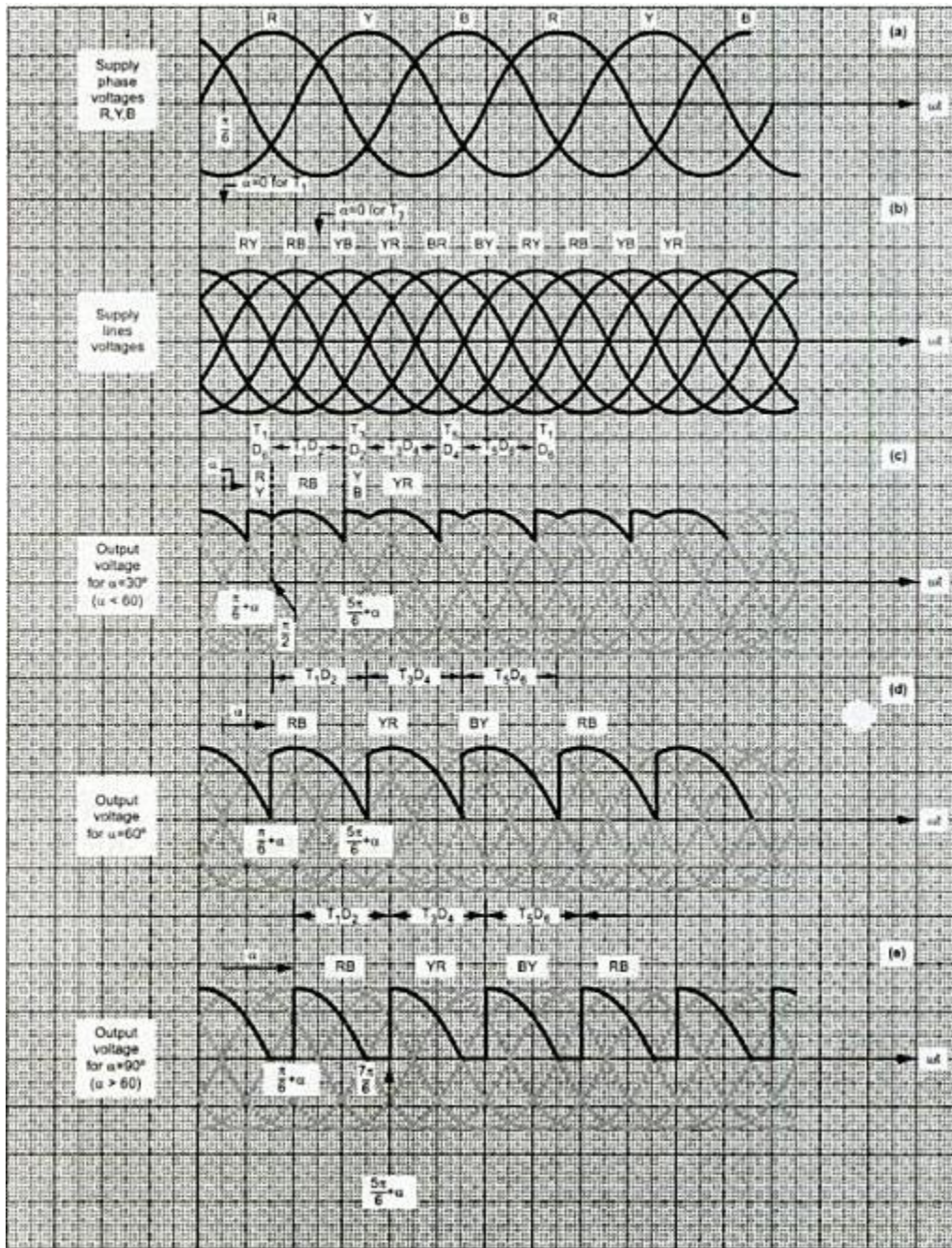


Fig 3: Wave Form of Three Phase half controlled bridge rectifier



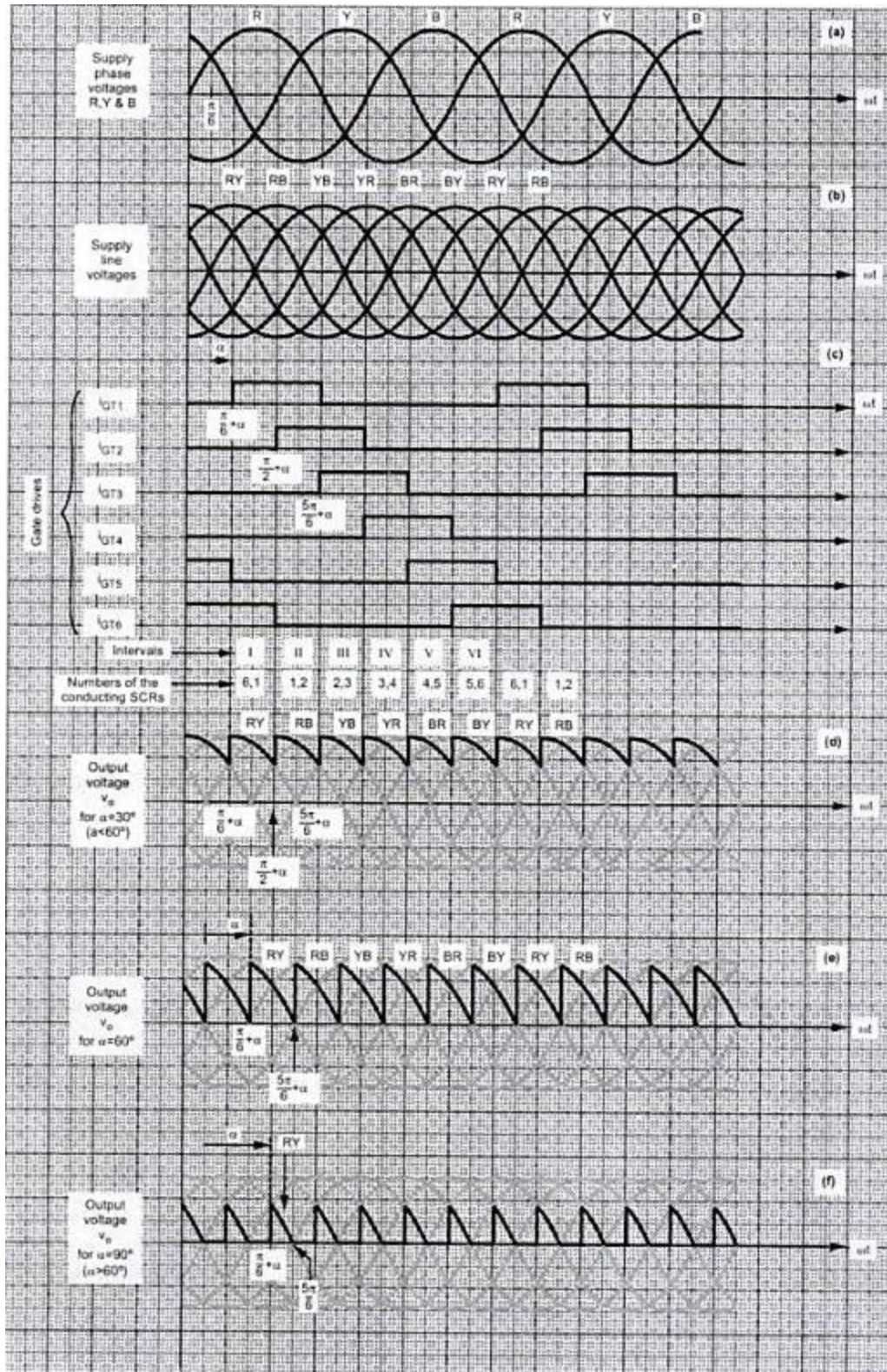



Fig 4: Waveform of Three Phase Fully Controlled Bridge Rectifier

**Theory:****THREE PHASE FULLY CONTROLLED CONVERTER**

A three phase fully controlled converter is obtained by replacing all the six diodes of an uncontrolled converter by six thyristors as shown in Fig 2. For any current to flow in the load at least one device from the top group ( $T_1, T_3, T_5$ ) and one from the bottom group ( $T_2, T_4, T_6$ ) must conduct. Like an uncontrolled converter only one device from these two groups will conduct.

Device Mode	$V_{T1}$	$V_{T2}$	$V_{T3}$	$V_{T4}$	$V_{T5}$	$V_{T6}$	$V_o$
$T_1T_2$	0	0	$v_{ba}$	$v_{ca}$	$v_{ca}$	$v_{cb}$	$v_{ac}$
$T_2T_3$	$v_{ab}$	0	0	$v_{ca}$	$v_{cb}$	$v_{cb}$	$v_{bc}$
$T_3T_4$	$v_{ab}$	$v_{ac}$	0	0	$v_{cb}$	$v_{ab}$	$v_{ba}$
$T_4T_5$	$v_{ac}$	$v_{ac}$	$v_{bc}$	0	0	$v_{ab}$	$v_{ca}$
$T_5T_6$	$v_{ac}$	$v_{bc}$	$v_{bc}$	$v_{ba}$	0	0	$v_{cb}$
$T_6T_1$	0	$v_{bc}$	$v_{ba}$	$v_{ba}$	$v_{ca}$	0	$v_{ab}$
NONE	-	-	-	-	-	-	E

Fig (a): Conduction Table

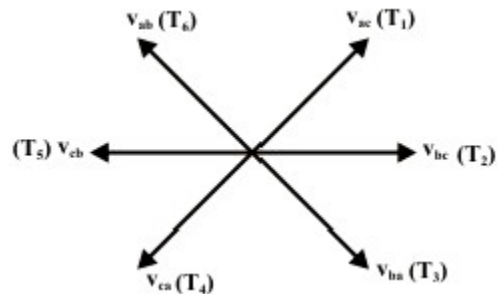

Fig(b): Phasor Diagram

Then from symmetry consideration we can see that each thyristor conducts for  $120^\circ$  of the input cycle. Now the thyristors are fired in the sequence  $T_1 \rightarrow T_2 \rightarrow T_3 \rightarrow T_4 \rightarrow T_5 \rightarrow T_6 \rightarrow T_1$  with  $60^\circ$  interval between each firing. Therefore thyristors on the same phase leg are fired at an interval of  $180^\circ$  and hence can not conduct simultaneously. This leaves only six possible conduction mode for the converter in the continuous conduction mode of operation. These are  $T_1T_2, T_2T_3, T_3T_4, T_4T_5, T_5T_6, T_6T_1$ . Each conduction mode is of  $60^\circ$  duration and appears in the sequence mentioned. The conduction table of Fig(a) shows voltage across different devices and the dc output voltage for each conduction interval. The phasor diagram of the line voltages appear in Fig. (b). Each of these line voltages can be associated with the firing of a thyristor with the help of the conduction table. For example the thyristor  $T_1$  is fired at the end of  $T_5T_6$  conduction interval. During this period the voltage across  $T_1$  was  $V_{ac}$ . Therefore  $T_1$  is fired  $\alpha$  angle after the positive going zero crossing of  $V_{ac}$ . Similar observation can be made about other thyristors. The phasor diagram of Fig (b) also confirms that all the thyristors are fired in the correct sequence with  $60^\circ$  interval between each firing.



## THREE PHASE HALF CONTROLLED CONVERTER

Fig:1 shows the circuit diagram of three phase half controlled converter supplying an R load. In the continuous conduction mode only one thyristor from top group and only one diode from the bottom group conduct at a time. However, unlike fully controlled converter here both devices from the same phase leg can conduct at the same time. Hence, there are nine conducting modes as shown in Fig (c).



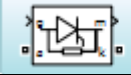
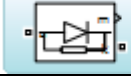
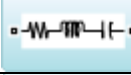

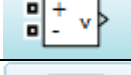
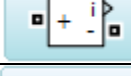

Mode Volt	T <sub>1</sub> D <sub>2</sub>	D <sub>2</sub> T <sub>3</sub>	T <sub>3</sub> D <sub>4</sub>	D <sub>4</sub> T <sub>5</sub>	T <sub>5</sub> D <sub>6</sub>	D <sub>6</sub> T <sub>1</sub>	T <sub>1</sub> D <sub>4</sub>	T <sub>3</sub> D <sub>6</sub>	T <sub>5</sub> D <sub>2</sub>
V <sub>T1</sub>	0	V <sub>ab</sub>	V <sub>ab</sub>	V <sub>ac</sub>	V <sub>ac</sub>	0	0	V <sub>ab</sub>	V <sub>ac</sub>
V <sub>D2</sub>	0	0	V <sub>ac</sub>	V <sub>ac</sub>	V <sub>bc</sub>	V <sub>bc</sub>	V <sub>ac</sub>	V <sub>bc</sub>	0
V <sub>T3</sub>	V <sub>ba</sub>	0	0	V <sub>bc</sub>	V <sub>bc</sub>	V <sub>ba</sub>	V <sub>ba</sub>	0	V <sub>bc</sub>
V <sub>D4</sub>	V <sub>ca</sub>	V <sub>ca</sub>	0	0	V <sub>ba</sub>	V <sub>ba</sub>	0	V <sub>ba</sub>	V <sub>ca</sub>
V <sub>T5</sub>	V <sub>ca</sub>	V <sub>cb</sub>	V <sub>cb</sub>	0	0	V <sub>ca</sub>	V <sub>ca</sub>	V <sub>cb</sub>	0
V <sub>D6</sub>	V <sub>cb</sub>	V <sub>cb</sub>	V <sub>ab</sub>	V <sub>ab</sub>	0	0	V <sub>ab</sub>	0	V <sub>cb</sub>
V <sub>0</sub>	V <sub>ac</sub>	V <sub>bc</sub>	V <sub>ba</sub>	V <sub>ca</sub>	V <sub>cb</sub>	V <sub>ab</sub>	0	0	0

Fig (c): Conduction Table

Now consider the conducting and blocking state of D<sub>2</sub>. In the blocking state the voltage across D<sub>2</sub> is either V<sub>ac</sub> or V<sub>bc</sub>. Hence, D<sub>2</sub> can block only when these voltages are negative. Taking V<sub>bc</sub> as the reference phasor (i.e.,  $V_{bc} = \sqrt{2}V_L \sin \omega t$ ) D<sub>2</sub> will block during  $2\pi/3 \leq \omega t \leq 2\pi$  and will conduct in the interval  $0 \leq \omega t \leq 2\pi/3$ . Similarly it can be shown that D<sub>4</sub> and D<sub>6</sub> will conduct during  $2\pi/3 \leq \omega t \leq 4\pi/3$  and  $4\pi/3 \leq \omega t \leq 2\pi$  respectively.

Next consider conduction of T<sub>1</sub>. The firing sequence of the thyristor is T<sub>1</sub> → T<sub>3</sub> → T<sub>5</sub>. Therefore before T<sub>1</sub> comes into conduction T<sub>5</sub> conducts and voltage across T<sub>1</sub> is  $V_{ac} = \sqrt{2}V_L \sin(\omega t + \pi/3)$ . If the firing angle of T<sub>1</sub> is  $\alpha$  then T<sub>1</sub> starts conduction at  $\omega t = \alpha - \pi/3$  and conducts upto  $\alpha + \pi/3$ . Similarly T<sub>3</sub> and T<sub>5</sub> conducts during  $\alpha + \pi/3 \leq \omega t \leq \alpha + \pi$  and  $\alpha + \pi \leq \omega t \leq 2\pi + \alpha - \pi/3$ .

**Procedure:**

Operation	Path	Icon
Opening Simulink	1. Click on the Simulink icon on Matlab taskbar 2. Type Simulink on Matlab Command Window	
Selecting New File	File -> New -> Model	
Selecting Source	Libraries -> SimpowerSystems -> electrical sources	 AC Voltage Source
Selecting Thyristor	Libraries -> SimPowerSystems -> PowerElectronics -> Thyristor	 Thyristor
Selecting Diode	Libraries -> SimPowerSystems -> PowerElectronics -> Diodes	 Diode
Selecting Series RLC branch	Libraries -> SimpowerSystems -> Elements	 Series RLC Load
Selecting Pulse Generater(Triggering)	Libraries -> Sources	 Pulse Generator
Voltage Measurement	Libraries -> SimpowerSystems -> Measurement	 Voltage Measurement
Current Mesurement	Libraries -> SimpowerSystems -> Measurement	 Current Measurement
Scope	Libraries -> Sink	 Scope

**RESULT:**

Three phase fully controlled and half controlled bridge rectifier is simulated and graphs are obtained.